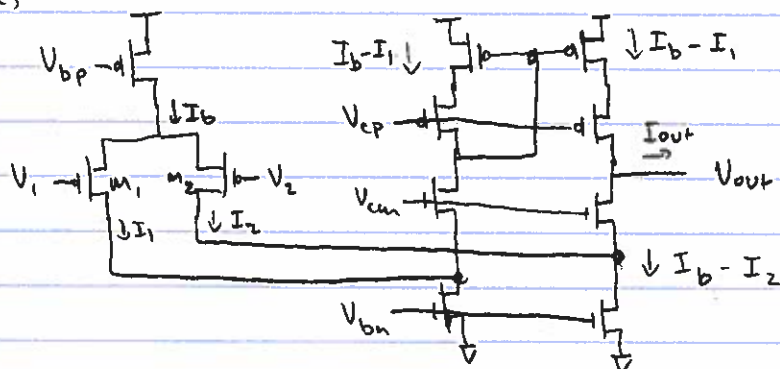



1) a)



$$I_{out} = (I_b - I_1) - (I_b - I_2) \Rightarrow \boxed{I_{out} = I_2 - I_1}$$

Since the differential pair is PMOS an increase in Voltage will decrease the current. Thus if we increase V_1 , then I_1 will decrease yielding a larger I_{out} . Conversely, if we increase V_2 , then I_2 will decrease yielding a smaller I_{out} . Therefore V_1 is the noninverting input and V_2 is the inverting input as explained above.

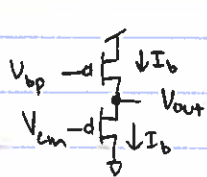b) Assume all transistors of strength 1 in PMOS drain follower



$$I_b = S I_s \log^2 \left(1 + e^{\frac{\kappa (V_{dd} - V_{bp}) - V_{To}}{V_{T0}}} \right) - \frac{(V_{dd} - V_{cm})}{2U_T}$$

$$= S I_s \log^2 \left(1 + e^{\frac{\kappa (V_{dd} - V_{cm}) - V_{To}}{V_{T0}}} \right) - \frac{(V_{dd} - V_{out})}{2U_T}$$

$$\Rightarrow \kappa (V_{dd} - V_{bp} - V_{To}) = \kappa (V_{dd} - V_{cm} - V_{To}) - (V_{dd} - V_{out})$$

$$\cancel{\kappa V_{dd}} - \cancel{\kappa V_{bp}} - \cancel{\kappa V_{To}} = \cancel{\kappa V_{dd}} - \cancel{\kappa V_{cm}} - \cancel{\kappa V_{To}} - V_{dd} + V_{out}$$

$$-\kappa V_{bp} = -\kappa V_{cm} - V_{dd} + V_{out}$$

$$V_{out} = V_{dd} + \kappa V_{cm} - \kappa V_{bp}$$

$$V_{out} = V_{dd} - \kappa (V_{bp} - V_{cm})$$

$$\therefore V_{dd} - V_{sosat} \geq V_{dd} - \kappa (V_{bp} - V_{cm}) \Rightarrow \frac{V_{sosat}}{\kappa} \leq V_{bp} - V_{cm} \Rightarrow -V_{cm} \geq \frac{V_{sosat}}{\kappa} - V_{bp}$$

$$\Rightarrow \underline{\underline{V_{cm} \leq V_{bp} - \frac{V_{sosat}}{\kappa}}}$$

- 1) b) (continued)
 We know that for M_6 to remain in saturation and conduct I_b the node voltage between M_6 , M_1 , and M_2 needs to be at least V_{gsat} below V_{dd} . Following the PMOS drain follower calculations before, this is the case when

$$V_{cm} \leq V_{bp} - \frac{V_{gsat}}{K_L} \quad \text{Thus, this is the maximum common}$$

mode voltage the circuit can handle, since this is a PMOS differential pair the minimum V_{cm} is 0V. It is important to note that this is a conservative estimate since only $\frac{W}{L} = 1$ transistors. If we were to consider the differential pair as $\frac{W}{L} = 2$, we would find a slightly higher allowable range for V_{cm} .

- c) Please refer to 1-a for explanation $I_{out} = I_2 - I_1$

d) The currents sunk by M_3 and M_4 need to be equal to I_b . If M_3 or M_4 were to sink less than I_b then if $I_1 = I_b$ current would need to flow upwards through the M_7 , M_9 , and M_5 branches. This would break the diode connection yielding a circuit that does not function properly. Similarly, if M_3 and M_4 were to sink more than I_b then small changes in I_1 and I_2 will not affect the output current as much (if $2I_b - \frac{I_b}{2}$ is a smaller change than $I_b - \frac{I_b}{2}$). This would, therefore, decrease the change in output current as well as the gain of the circuit for that reason. Thus, M_3 and M_4 must sink I_b .

e)

